

Digital Logic Design

Ch 2

Combinational Logic

Topics

- Combinational logic definition
- Axioms and Theorems of Boolean algebra
- Realizing Boolean formulas
- Levels of logic expressions
 - ▣ Two-level logic
 - ▣ Canonical forms
 - ▣ Multi-level logic
- Simplifying two-level logic expressions
 - ▣ Boolean cubes
 - ▣ Karnaugh maps

Combinational logic

- Define
 - ▣ the kind of digital system whose output behavior depends only on the current inputs → each output is defined as a function (combination) of inputs
 - ▣ memoryless: its outputs are independent of the historical sequence of values presented to it as inputs
 - ▣ (cf.) sequential logic
- Many ways to describe combination logic
 - ▣ Boolean algebra expression
 - ▣ wired up logic gates
 - ▣ truth tables tabulating input and output combinations
 - ▣ graphical maps
 - ▣ program statements in a hardware description language

Examples of combinational logic

□ The equivalence circuit

X	Y	Equal
0	0	1
0	1	0
1	0	0
1	1	1

□ The tally circuit

X	Y	Zero	One	Two
0	0	1	0	0
0	1	0	1	0
1	0	0	1	0
1	1	0	0	1

□ Binary Adder

X	Y	Cout	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

< Half-adder >

X	Y	Cin	Cout	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

< Full-adder >

Laws and theorems of Boolean logic

□ Basic concept

- Boolean algebra is the mathematical foundation of digital systems
- laws (axioms) : the properties to which the operations of Boolean algebra must adhere
- axioms can be used to prove more general laws

□ Boolean operations

- operation order

COMPLEMENT \rightarrow AND \rightarrow OR

- parentheses : change the default order of evaluation
- examples :
1) $\overline{A} \bullet B + C = ((\overline{A}) \bullet B) + C$

Axioms of Boolean algebra

- A Boolean algebra consists of
 - ▣ a set of elements B
 - ▣ binary operations $\{ +, \cdot \}$
 - ▣ and a unary operation $\{ ' \}$
 - ▣ such that the following axioms hold (Huntington's postulates):

- Axioms

A1. the set B contains at least two elements: a, b

A2. closure: $a + b$ is in B

$a \cdot b$ is in B

A3. commutativity: $a + b = b + a$

$a \cdot b = b \cdot a$

A4. associativity: $a + (b + c) = (a + b) + c$
 $= a + b + c$

$a \cdot (b \cdot c) = (a \cdot b) \cdot c$
 $= a \cdot b \cdot c$

A5. identity: $a + 0 = a$

$a \cdot 1 = a$

A6. distributivity: $a + (b \cdot c) = (a + b) \cdot (a + c)$

$a \cdot (b + c) = (a \cdot b) + (a \cdot c)$

A7. complementarity: $a + a' = 1$

$a \cdot a' = 0$

Theorems of Boolean algebra

- Operations with 0 and 1 (Unit/Zero properties)

1. $X + 0 = X$

1D. $X \bullet 1 = X$

2. $X + 1 = 1$

2D. $X \bullet 0 = 0$

- Idempotent theorem:

3. $X + X = X$

3D. $X \bullet X = X$

- Involution theorem:

4. $(X')' = X$

- Theorem of complementarity:

5. $X + X' = 1$

5D. $X \bullet X' = 0$

- Commutative law:

6. $X + Y = Y + X$

6D. $X \bullet Y = Y \bullet X$

- Associative law:

7. $(X + Y) + Z = X + (Y + Z)$
 $= X + Y + Z$

7D. $(X \bullet Y) \bullet Z = X \bullet (Y \bullet Z)$
 $= X \bullet Y \bullet Z$

Theorems of Boolean algebra

□ Distributive law:

$$8. X \bullet (Y + Z) = (X \bullet Y) + (X \bullet Z) \quad 8D. X + (Y \bullet Z) = (X + Y) \bullet (X + Z)$$

□ Simplification theorems:

$$9. X \bullet Y + X \bullet Y' = X$$

$$9D. (X + Y) \bullet (X + Y') = X$$

$$10. X + X \bullet Y = X$$

$$10D. X \bullet (X + Y) = X$$

$$11. (X + Y') \bullet Y = X \bullet Y$$

$$11D. (X \bullet Y') + Y = X + Y$$

□ DeMorgan's law:

$$12. (X + Y + Z + \dots)' \\ = X' \bullet Y' \bullet Z' \bullet \dots$$

$$12D. (X \bullet Y \bullet Z \bullet \dots)' \\ = X' + Y' + Z' + \dots$$

□ General form:

$$13. \{f(X_1, X_2, \dots, X_n, 0, 1, +, \bullet)\}' = \{f(X_1', X_2', \dots, X_n', 1, 0, \bullet, +)\}$$

Theorems of Boolean algebra

□ Duality:

$$14. (X + Y + Z + \dots)^D \\ = X \cdot Y \cdot Z \cdot \dots$$

$$14D. (X \cdot Y \cdot Z \cdot \dots)^D \\ = X + Y + Z + \dots$$

□ General form:

$$15. \{f(X_1, X_2, \dots, X_n, 0, 1, +, \cdot)\}^D = f(X_1, X_2, \dots, X_n, 1, 0, \cdot, +)$$

□ Theorem for multiplying and factoring

$$16. (X + Y) \cdot (X' + Z)$$

$$16D. X \cdot Y + X' \cdot Z = (X + X')(X + Z)(X' + Y)(Y + Z) \\ = (X + Z) \cdot (X' + Y)$$

$$= \underline{XX' + XZ + X'Y + YZ} = X \cdot Z + X' \cdot Y \quad \xrightarrow{\text{red arrow}} \quad X \Rightarrow Z$$

□ Consensus theorem:

$$17. X \cdot Y + Y \cdot Z + X' \cdot Z \\ = X \cdot Y + X' \cdot Z$$

$$17D. (X + Y) \cdot (Y + Z) \cdot (X' + Z) \\ = (X + Y) \cdot (X' + Z)$$

$$\text{Proof} \rightarrow XY + X'Z + YZ = XY + X'Z + (X + X')YZ = XY + X'Z + XYZ + X'YZ = X(Y + YZ) + X'(Z + YZ)$$

Verifying the Boolean theorems

- Verifying the theorems using the axioms of Boolean algebra

- Proving the uniting theorem(9): **$X \bullet Y + X \bullet Y' = X$**

Distributive law (8)	$X \bullet (Y + Y')$	$= X$
----------------------	----------------------	-------

Complementarity theorem (5)	$X \bullet (1)$	$= X$
-----------------------------	-----------------	-------

Identity (1D)	X	$= X$
---------------	-----	-------

- Proving the simplification theorem(10): **$X + X \bullet Y = X$**

Identity (1D)	$X \bullet 1 + X \bullet Y$	$= X$
---------------	-----------------------------	-------

Distributive law (8)	$X(1 + Y)$	$= X$
----------------------	------------	-------


Identity (2)	$X(1)$	$= X$
--------------	--------	-------

Identity (1)	X	$= X$
--------------	-----	-------

Duality vs. DeMorgan's law

□ Duality

 - a dual of a Boolean expression is derived by replacing
 - by +, + by •, 0 by 1, and 1 by 0, and leaving variables unchanged
- Any theorem that can be proven is thus also proven for its dual!



- A meta-theorem (a theorem about theorems) that allow to derive new theorems: (e.g.) the dual of the uniting theorem(9), $X \bullet Y + X \bullet Y' = X$, is $(X + Y) \bullet (X + Y') = X$. \Rightarrow The proof of the dual follows step-by-step, simply using the duals of the laws used in the original proof.

$$(X + Y) \bullet (X + Y') = X?$$

$$X + (Y \bullet Y') = X$$

Distributive law (8D)

$$X + 0 = X$$

Complementarity theorem (5D)


$$X = X$$

Identity (1)

Duality vs. DeMorgan's law

□ DeMorgan's law

 - $(a+b)' \equiv a'b'$
 $(ab)' \equiv a'+b'$



- give a procedure for complementing a complex function
- the complemented expression is derived by replacing all literals by their complements, 0 by 1, 1 by 0, \bullet by $+$ and $+$ by \bullet

- (e.g.) the complement of $Z = \bar{A}\bar{B}C + \bar{A}BC + A\bar{B}C + ABC$

$$\bar{Z} = \overline{(\bar{A}\bar{B}C + \bar{A}BC + A\bar{B}C + ABC)}$$

$$\bar{Z} = \overline{\bar{A}\bar{B}C} \cdot \overline{\bar{A}BC} \cdot \overline{A\bar{B}C} \cdot \overline{ABC}$$

$$\bar{Z} = (A + B + \bar{C}) (A + \bar{B} + \bar{C}) (\bar{A} + B + \bar{C}) (\bar{A} + \bar{B} + C)$$



Possible logic functions of two variables

- There are 16 possible functions of 2 input variables:




X	Y	16 possible functions (F0–F15)															
0	0	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1
0	1	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1	0	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1
		<div> <div>0</div> <div>X and Y</div> <div>NOT (X implies Y)</div> </div> <div> <div>X</div> <div>NOT (Y implies X)</div> </div> <div> <div>Y</div> <div>X or Y</div> </div> <div> <div>X xor Y</div> <div>X nor Y</div> <div>not (X or Y)</div> </div> <div> <div>X = Y</div> <div>Y implies X</div> <div>X implies Y</div> </div> <div> <div>not Y</div> <div>not X</div> <div>X nand Y</div> <div>not (X and Y)</div> </div> <div>1</div>															

Cost of different logic functions

  - Different functions are cheaper or more expensive to implement in CMOS technology
 - ▣ Each has a cost associated with the number of switches needed
 - ▣ 0 (F0) and 1 (F15): require **0** switches, directly connect output to low/high
 - ▣ X (F3) and Y (F5): require **0** switches, output is one of inputs
 - ▣ X' (F12) and Y' (F10): require **2** switches for "inverter" or NOT-gate
 - ▣ $X \text{ nor } Y$ (F4) and $X \text{ nand } Y$ (F14): require **4** switches
 - ▣ $X \text{ or } Y$ (F7) and $X \text{ and } Y$ (F1): require **6** switches → 
 - ▣ $X = Y$ (F9) and $X \oplus Y$ (F6): require **16** switches → 
- Thus...
 - ▣ A simpler expression for a Boolean function does not necessarily minimize the number of transistors for its realization.
 - ▣ Because NOT, NOR, and NAND are the cheapest, they are the functions that we implement the most in practice.


Realizing Boolean formulas: logic gates

□ NAND

 


X	Y	Z
0	0	1
0	1	1
1	0	1
1	1	0

□ NOR

 

X	Y	Z
0	0	1
0	1	0
1	0	0
1	1	0


□ XOR
 $X \oplus Y$

 

X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	0

$X \text{ xor } Y = X Y' + X' Y$
X or Y but not both
("inequality", "difference")

□ XNOR
 $X = Y$



 


X	Y	Z
0	0	1
0	1	0
1	0	0
1	1	1

$X \text{ xnor } Y = X Y + X' Y'$
X and Y are the same
("equality", "coincidence")


Realizing Boolean formulas: logic blocks & hierarchy

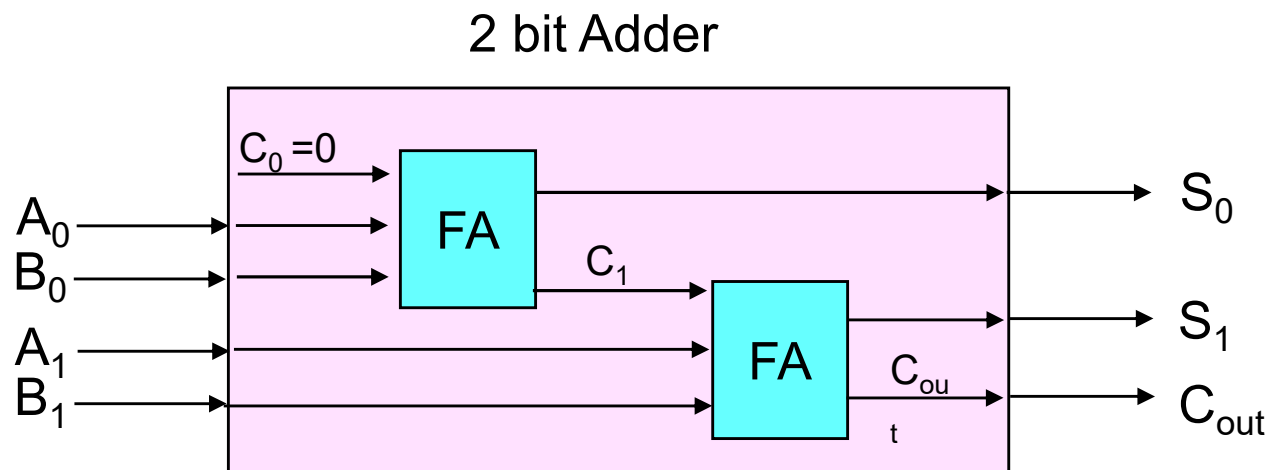  - Complex logic function can be constructed from more primitive functions by wiring up logic gates
- example : 2-bit adder




Time behavior and waveforms

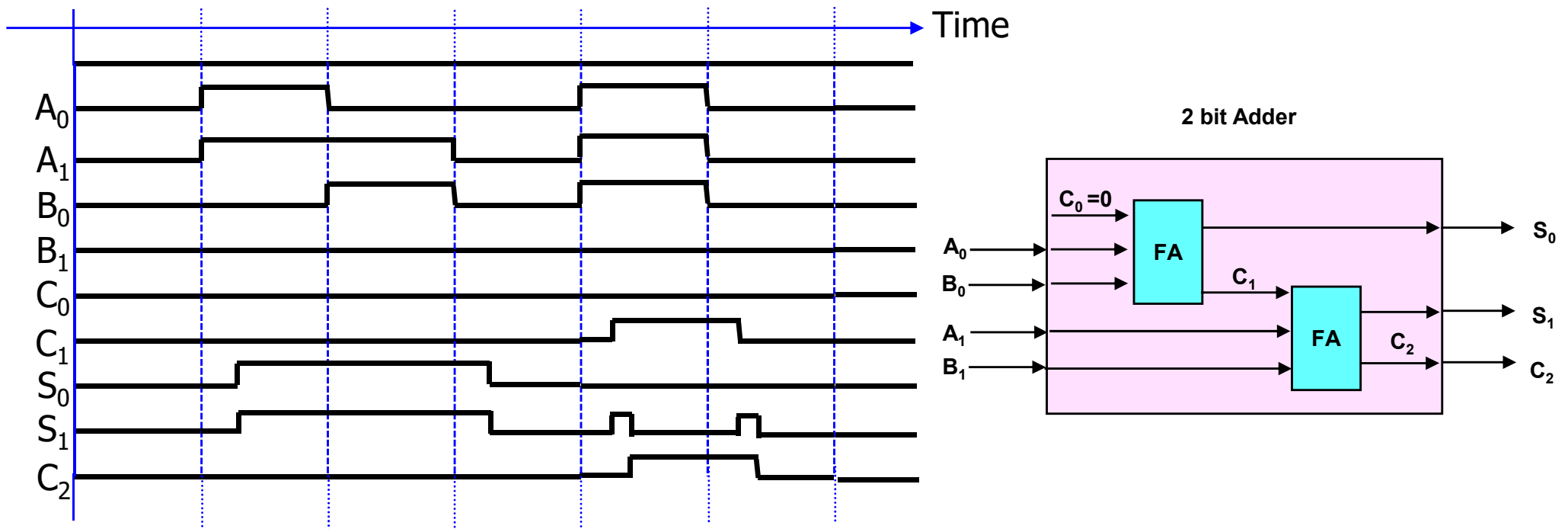- Waveform: represent signal propagation over time
 - ▣ x-axis: the time step
 - ▣ y-axis: the logical value
- Unit delay model: considering the delay through any gate as taking exactly one time unit for a simplifying assumption



Minimizing the number of gates & wires

A	B	C	Z
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

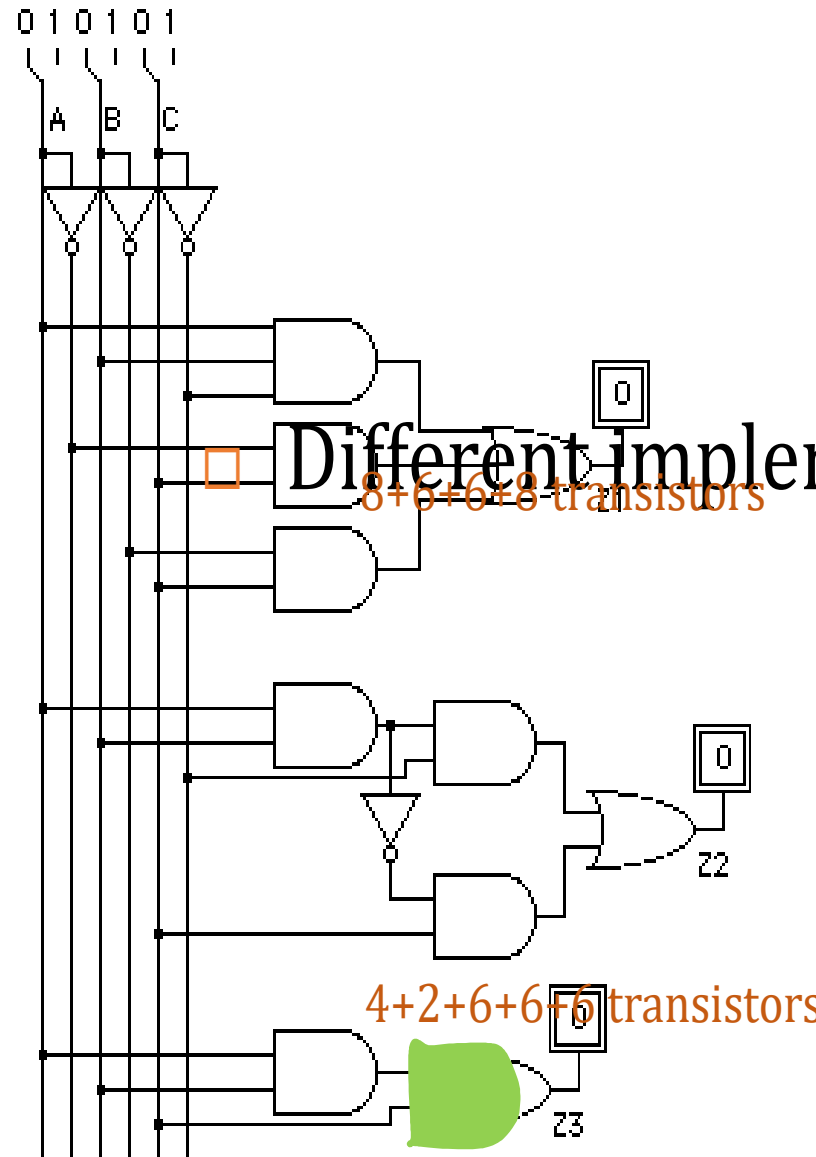


Different implementations of one f

$$= ABC' + (A' + B')C$$

$$= ABC' + (AB)'C$$

4+2+6+6+6 transistors

on

 

Two-level logic

- Nested levels to express Boolean logics
 - ▣ One-level: $Z = A + B$, $F = AB'$, $G = A'B$
 - ▣ Two-level: $Y = F + G = AB' + A'B$
- Two-level are sufficient to represent any Boolean expression.
 - ▣ **Canonical form:** standard form to represent a Boolean expression
 - ▣ unique algebraic signature of the function
- Two alternative canonical forms
 - ▣ sum-of-products: $AB' + A'B$
 - ▣ product-of-sums: $(A + B')(A' + B)$
- Incompletely specified function
 - ▣ In the original form, all 2^n possible input combinations must be considered for a function with n inputs.
 - ▣ For flexibility, we consider one more set: don't care set

Sum-of-products canonical forms

- a.k.a. *minterm expansion* or a *disjunctive normal form* (**DNF**)
- An expression in DNF consists of an ORed list of minterms.

			F =		001	011	101	110	111
			F =		A'B'C	+ A'BC	+ AB'C	+ ABC'	+ ABC
A	B	C	F	F'					
0	0	0	0	1					
0	0	1	1	0					
0	1	0	0	1					
0	1	1	1	0					
1	0	0	0	1					
1	0	1	1	0					
1	1	0	1	0					
1	1	1	1	0					

F' = A'B'C' + A'BC' + AB'C'


Sum-of-products canonical forms

□ Product term (or minterm)

- ▣ ANDed product of literals – input combination for which output is true
- ▣ each variable appears exactly once, true or inverted (but not both)

A	B	C	minterms	
0	0	0	$A'B'C'$	m0
0	0	1	$A'B'C$	m1
0	1	0	$A'BC'$	m2
0	1	1	$A'BC$	m3
1	0	0	$AB'C'$	m4
1	0	1	$AB'C$	m5
1	1	0	ABC'	m6
1	1	1	ABC	m7

short-hand notation for
minterms of 3 variables



F in canonical form:

$$\begin{aligned}F(A, B, C) &= \Sigma m(1,3,5,6,7) \\&= m1 + m3 + m5 + m6 + m7 \\&= A'B'C + A'BC + AB'C + ABC' + ABC\end{aligned}$$

canonical form \neq minimal form

$$\begin{aligned}F(A, B, C) &= A'B'C + A'BC + AB'C + ABC + ABC' \\&= (A'B' + A'B + AB' + AB)C + ABC' \\&= ((A' + A)(B' + B))C + ABC' \\&= C + ABC' \\&= ABC' + C \\&= AB + C\end{aligned}$$

Product-of-sums canonical forms

- a.k.a, *maxterm expansion* or a *conjunctive normal form* (CNF)
- An expression in CNF consists of an ANDed list of maxterms

A	B	C	F	F'
0	0	0	0	1
0	0	1	1	0
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0

$$F = \overset{000}{(A + B + C)} \overset{010}{(A + B' + C)} \overset{100}{(A' + B + C)}$$

$$F' = (A + B + C') (A + B' + C') (A' + B + C') (A' + B' + C) (A' + B' + C')$$

Product-of-sums canonical forms

□ Sum term (or maxterm)

- ▣ ORed sum of literals – input combination for which output is false
- ▣ each variable appears exactly once, true or inverted (but not both)

A	B	C	maxterms	
0	0	0	$A+B+C$	M0
0	0	1	$A+B+C'$	M1
0	1	0	$A+B'+C$	M2
0	1	1	$A+B'+C'$	M3
1	0	0	$A'+B+C$	M4
1	0	1	$A'+B+C'$	M5
1	1	0	$A'+B'+C$	M6
1	1	1	$A'+B'+C'$	M7


F in canonical form:

$$\begin{aligned}
 F(A, B, C) &= \prod M(0,2,4) \\
 &= M0 \cdot M2 \cdot M4 \\
 &= (A + B + C) (A + B' + C) (A' + B + C)
 \end{aligned}$$

canonical form \neq minimal form

$$\begin{aligned}
 F(A, B, C) &= (A + B + C) (A + B' + C) (A' + B + C) \\
 &= (A + B + C) (A + B' + C) \\
 &\quad (A + B + C) (A' + B + C) \\
 &= (A + C) (B + C)
 \end{aligned}$$

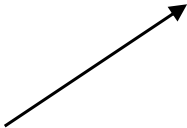short-hand notation for
maxterms of 3 variables



S-o-P, P-o-S and DeMorgan's law

□ Sum-of-products

- $F' = A'B'C' + A'BC' + AB'C'$

□ Apply DeMorgan's

- $(F')' = (A'B'C' + A'BC' + AB'C')'$

- $F = (A + B + C) (A + B' + C) (A' + B + C)$

□ Product-of-sums


- $F' = (A + B + C') (A + B' + C') (A' + B + C') (A' + B' + C) (A' + B' + C')$

□ Apply DeMorgan's

- $(F')' = ((A + B + C')(A + B' + C')(A' + B + C')(A' + B' + C)(A' + B' + C'))'$

- $F = A'B'C + A'BC + AB'C + ABC' + ABC$

 4 alternative two-level implementations of F



Note

$$A + A' = 1$$

$$A'B' + A'B + AB' + AB = 1$$

canonical sum-of-products

$$F1 = A'B'C + A'BC + AB'C + ABC' + ABC$$

minimized sum-of-products

$$F2 = AB + C$$

$$= ((AB+C)')' = ((A'+B')C')'$$

$$= (A'C' + B'C')$$

canonical product-of-sums

$$F3 = (A + B + C)(A + B' + C)(A' + B + C)$$

minimized product-of-sums

$$F4 = (A + C)(B + C)$$

Conversion between canonical forms

- Minterm to maxterm conversion
 - ▣ use maxterms whose indices do not appear in DNF
 - ▣ e.g., $F(A,B,C) = \Sigma m(1,3,5,6,7) = \Pi M(0,2,4)$
- Maxterm to minterm conversion
 - ▣ use minterms whose indices do not appear in CNF
 - ▣ e.g., $F(A,B,C) = \Pi M(0,2,4) = \Sigma m(1,3,5,6,7)$
- DNF of F to DNF of F'
 - ▣ use minterms whose indices do not appear
 - ▣ e.g., $F(A,B,C) = \Sigma m(1,3,5,6,7)$ $F'(A,B,C) = \Sigma m(0,2,4)$
- CNF of F to CNF of F'
 - ▣ use maxterms whose indices do not appear
 - ▣ e.g., $F(A,B,C) = \Pi M(0,2,4)$ $F'(A,B,C) = \Pi M(1,3,5,6,7)$

Incompletely specified functions

- Example: *binary coded decimal* (BCD) increment by 1
 - ▣ BCD digits encode the decimal digits 0 – 9
in the bit patterns 0000 – 1001

A	B	C	D	W	X	Y	Z	
0	0	0	0	0	0	0	1	
0	0	0	1	0	0	1	0	off-set of W
0	0	1	0	0	0	1	1	
0	0	1	1	0	1	0	0	on-set of W
0	1	0	0	0	1	0	1	
0	1	0	1	0	1	1	0	don't care (DC) set of W
0	1	1	0	0	1	1	1	
0	1	1	1	1	0	0	0	
1	0	0	0	1	0	0	1	
1	0	0	1	0	0	0	0	
1	0	1	0	X	X	X	X	these inputs patterns should never be encountered in practice – "don't care" about associated output values, can be exploited in minimization
1	0	1	1	X	X	X	X	
1	1	0	0	X	X	X	X	
1	1	0	1	X	X	X	X	
1	1	1	0	X	X	X	X	
1	1	1	1	X	X	X	X	
1	1	1	1	X	X	X	X	

Notation for incompletely specified functions

- Don't cares and canonical forms
 - ▣ so far, only represented on-set
 - ▣ also represent don't-care-set
 - ▣ need two of the three sets (on-set, off-set, dc-set)
- Canonical representations of the BCD increment by 1 function:
 - ▣ $Z = m_0 + m_2 + m_4 + m_6 + m_8$
 $+ d_{10} + d_{11} + d_{12} + d_{13} + d_{14} + d_{15}$
 $= \Sigma [m(0,2,4,6,8) + d(10,11,12,13,14,15)]$
 - ▣ $Z = M_1 \cdot M_3 \cdot M_5 \cdot M_7 \cdot M_9$
 $\cdot D_{10} \cdot D_{11} \cdot D_{12} \cdot D_{13} \cdot D_{14} \cdot D_{15}$
 $= \Pi [M(1,3,5,7,9) \cdot D(10,11,12,13,14,15)]$
 - ▣ For realization of Z, don't care terms will be eventually assigned 0 or 1 in a way to simplify the circuit of Z as much as possible.

A	B	C	D	W	X	Y	Z
0	0	0	0	0	0	0	1
0	0	0	1	0	0	1	0
0	0	1	0	0	0	1	1
0	0	1	1	0	1	0	0
0	1	0	0	0	1	0	1
0	1	0	1	0	1	1	0
0	1	1	0	0	1	1	1
0	1	1	1	1	0	0	0
1	0	0	0	1	0	0	1
1	0	0	1	0	0	0	0
1	0	1	0	X	X	X	X
1	0	1	1	X	X	X	X
1	1	0	0	X	X	X	X
1	1	0	1	X	X	X	X
1	1	1	0	X	X	X	X
1	1	1	1	X	X	X	X

Simplification: 2-level combinational logic

- Finding a minimal S-of-P or P-of-S realization
- Algebraic simplification
 - ▣ not an algorithmic/systematic procedure
 - ▣ how do you know when the minimum realization has been found?
- Computer-aided design tools
 - ▣ precise solutions require very long computation times, especially for functions with many inputs (> 10)
 - ▣ heuristic methods employed – "educated guesses" to reduce amount of computation and yield good if not best solutions
- Hand methods still relevant
 - ▣ to understand automatic tools and their strengths and weaknesses
 - ▣ ability to check results (on small examples)

Essence of Boolean simplification

- Key tool to simplification: the **Uniting** theorem

$$\rightarrow AB' + AB = A(B' + B) = A$$

- Essence of simplification of two-level logic with uniting

- ▣ Find two element subsets of the ON-set where only one variable changes its value
- ▣ This single varying variable can be eliminated and a single product term used to represent both elements

$$F = A'B' + AB' = (A' + A)B' = B'$$

A	B	F
0	0	1
0	1	0
1	0	1
1	1	0





B has the same value in both on-set rows
– B remains

A has a different value in the two rows
– A is eliminated

Boolean cubes

abbreviated as ***n-cube***

    - Visual technique for identifying when the uniting theorem can be applied
- truth table with n input variables = *n-dimensional cube*




Mapping truth tables onto Boolean cubes

- The uniting theorem combines two **faces** of a cube into one larger face
- Adjacency plane
 - ▣ circled elements of the on-set that are directly adjacent
 - ▣ each adjacency plane corresponds to a product term
- Example:

A	B	G
0	0	1
0	1	0
1	0	1
1	1	0

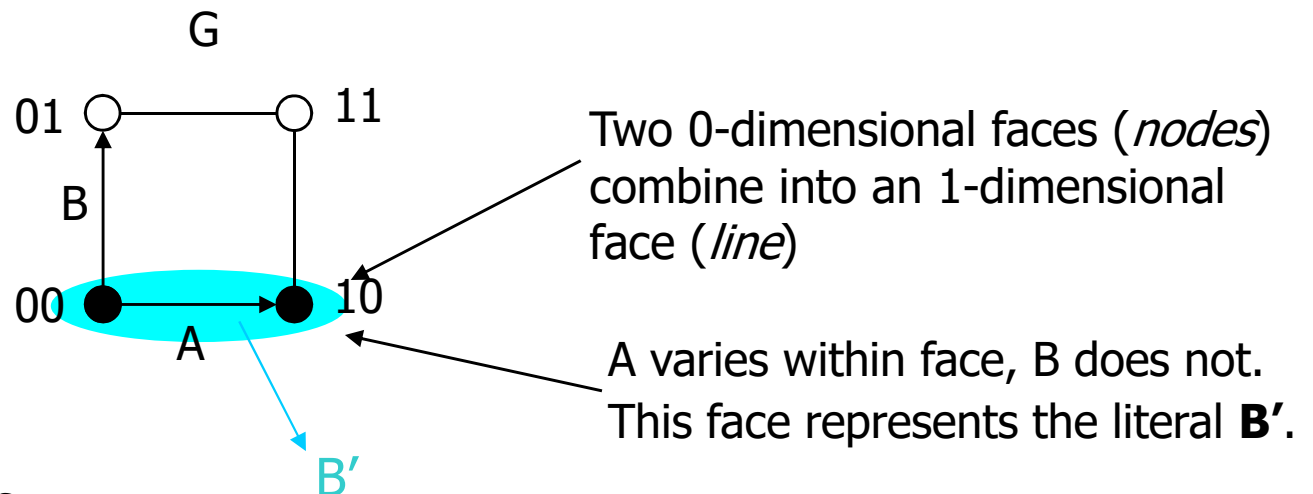ON-set = solid nodes
OFF-set = empty nodes
DC-set = ×'d nodes




Three variable example

Three 1-dimensional adjacency planes

□ Binary full-adder carry-out logic

A	B	C _{in}	C _{out}
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

 

The on-set is completely covered by the combination (OR) of the subcubes of lower dimensionality - note that "111" is covered three times.

$$C_{out} = BC_{in} + AB + AC_{in}$$



Four nodes (0-dimensional) are combined into three lines (1-dimensional)

Higher dimensional cubes


- Sub-cubes of higher dimension than 1
- Example: 2-dimensional adjacency plane in a 3-cube

$$F(A,B,C) = \sum m(4,5,6,7)$$

On-set forms a square
i.e., a cube of dimension 2

*represents an expression in one variable
i.e., 3 dimensions – 2 dimensions*

 A is asserted (true) and unchanged
B and C vary




This subcube represents the
literal A

*Four nodes (dimension 0) are
combined into four lines (dimension 1),
which are then combined into one 2-
dimensional sub-cube (square)*



$$\begin{aligned} &AB'C' + ABC' + AB'C + ABC \\ &= AB + AB' + AC + AC' \\ &= A \end{aligned}$$

m-cubes in n-dimensional Boolean space

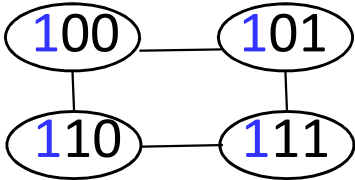- In a 3-cube (three variables):
 - ▣ 0-dimensional plane, i.e., a single **node**, yields a term in 3 literals
 - example : $\textcircled{101} = AB'C$
 - ▣ 1-dimensional plane, i.e., a **line** of two nodes, yields a term in 2 literals
 - example : $\textcircled{100} - \textcircled{101} = AB'$
 - ▣ 2-dimensional plane, i.e., a **squire** plane of four nodes, yields a term in 1 literal
 - example :  $\textcircled{100} - \textcircled{101} - \textcircled{110} - \textcircled{111} = A$
 - ▣ 3-dimensional plane, i.e., a **cube** of eight nodes, yields 0 literal meaning a constant logic "1"
- In general, an **m**-dimensional adjacency plane within an **n**-dimensional cube ($m < n$) yields a term with **$n - m$** literals

Karnaugh maps

- The cube notation provides visual clues as to where the uniting theorem is applied to elements of on-set.
- But, humans have the difficulty of visualizing adjacencies in more than 3 dimensional cubes.
- Karnaugh maps alternative reformulation of the truth table
 - ▣ for expressions at least up to **six** variables
 - ▣ wrap-around at edges
 - ▣ On-set elements with only one variable changing value are adjacent unlike the situation in a linear truth-table

B \ A	0	1
0	1 0	1 2
1	0 1	0 3

A	B	F
0	0	1
0	1	0
1	0	1
1	1	0

Karnaugh maps (K-Maps)

- Numbering scheme based on Gray-code
 - ▣ e.g., 00, 01, 11, 10 (for every advancement, a single bit changes)
 - ▣ only a single bit changes in code for adjacent map cells

000
001
011
010
110
111
101
100

		A			
		AB			
C	0	00	01	11	10
	1	0	2	6	4
C	1	1	3	7	5
		B			

		A			
		0	2	6	4
C	1	1	3	7	5
		B			




		A		
	0	4	12	8
	1	5	13	9
C	3	7	15	11
	2	6	14	10
		B		

K-map for *six* (=3+3) variables is possible
How about 7 or 8 variables?

$$13 = 1101 = ABC'D$$

Adjacencies in K-Maps

   - Wrap from first to last column
- Wrap top row to bottom row




Karnaugh map examples

□ 2-variable maps


▣ $F = AB' + AB = A$

A	B	F
0	0	0
0	1	0
1	0	1
1	1	1

 

▣ $G = A'B' + AB' = B'$

A	B	G
0	0	1
0	1	0
1	0	1
1	1	0

 


Karnaugh map examples

□ 3-variable maps


▣ full adder

A	B	C_{in}	C_{out}
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

 

$$AB + Bc_{in} + AC_{in}$$

□ $F(A,B,C) = \Sigma m(0,4,5,7)$

 

$$AC + B'C' + AB'$$

obtain the complement of the function by covering 0s with subcubes (see next page)

More K-Map examples

		A		
	0	0	1	1
C	0	0	1	1
	B			

$$G(A,B,C) = A$$

		A		
	1	0	0	1
C	0	0	1	1
	B			

$$F(A,B,C) = \sum m(0,4,5,7) = AC + B'C'$$

		A		
	0	1	1	0
C	1	1	0	0
	B			



Complement of $F(A,B,C) = \sum m(0,4,5,7)$
 F' simply replace 1's with 0's and vice versa

$$F'(A,B,C) = \sum m(1,2,3,6) = BC' + A'C$$

Karnaugh map: 4-variable example

□ $F(A,B,C,D) = \Sigma m(0,2,3,5,6,7,8,10,11,14,15)$

$$F = C + A'BD + B'D'$$

  

find the smallest number of the largest possible
subcubes to cover the On-set
(fewer terms with fewer inputs per term)

Karnaugh maps: don't cares

□ $f(A,B,C,D) = \Sigma m(1,3,5,7,9) + d(6,12,13)$

▣ without don't cares

■ $f = A'D + B'C'D$

		A			
		0	0	X	0
C		1	1	X	1
		1	1	0	0
		0	X	0	0
		B		D	

Karnaugh maps: don't cares

□ $f(A,B,C,D) = \Sigma m(1,3,5,7,9) + d(6,12,13)$

▣ $f = A'D + B'C'D$

without don't cares

▣ $f = A'D + C'D$

with don't cares

	A			
	0	0	X	0
	1	1	X	1
	1	1	0	0
C	0	X	0	0
	B			

D

by using don't care as a "1"
a 2-cube can be formed
rather than a 1-cube to cover
this node

don't cares can be treated as
1s or 0s
depending on which is more
advantageous

Multilevel Logic

□ Comparison with 2-level logic

- ▣ gain: reduce the number of wires, gates and inputs to each gate
- ▣ lose: add up more combined delay due to the increased levels of logic

□ Example

▣ 2-level logic

$$Z = ADF + AEF + BDF + BEF + CDF + CEF + G$$

→ six 3-input AND gates, one 7-input OR gate

▣ multilevel logic

$$Z = (AD + AE + BD + BE + CD + CE)F + G$$

$$Z = [(A + B + C)D + (A + B + C)E]F + G$$

$$Z = (A + B + C)(D + E)F + G$$

→ one 3-input OR gate, two 2-input OR gates, one 3-input AND gate

Chapter review

- Variety of primitive logic building blocks
 - ▣ NOT, AND, OR, NAND, NOR, XOR and XNOR gates
- Axioms and theorems of Boolean algebra
 - ▣ proofs by re-writing and perfect induction
- Two-level logic
 - ▣ canonical forms: sum-of-products and product-of-sums
 - ▣ incompletely specified functions
- Simplification
 - ▣ a start at understanding two-level simplification
 - ▣ Boolean cubes
 - ▣ K-Map